

Digital Design LA1 (10 Marks)

Your email address (1nt19is122.raghunathan@nmit.ac.in) will be recorded when you submit this form. Not you? [Switch account](#)

* Required

MCQ Questions

Each Carries 1 marks

*


A circuit outputs a digit in the form of 4 bits. 0 is represented by 0000, 1 by 0001, ..., 9 by 1001. A combinational circuit is to be designed which takes these 4 bits as input and outputs 1 if the digit ≥ 5 , and 0 otherwise. If only AND, OR and NOT gates may be used, what is the minimum number of gates required?

- ☒ 3
- ☐ 5
- ☐ 2
- ☐ 4



*

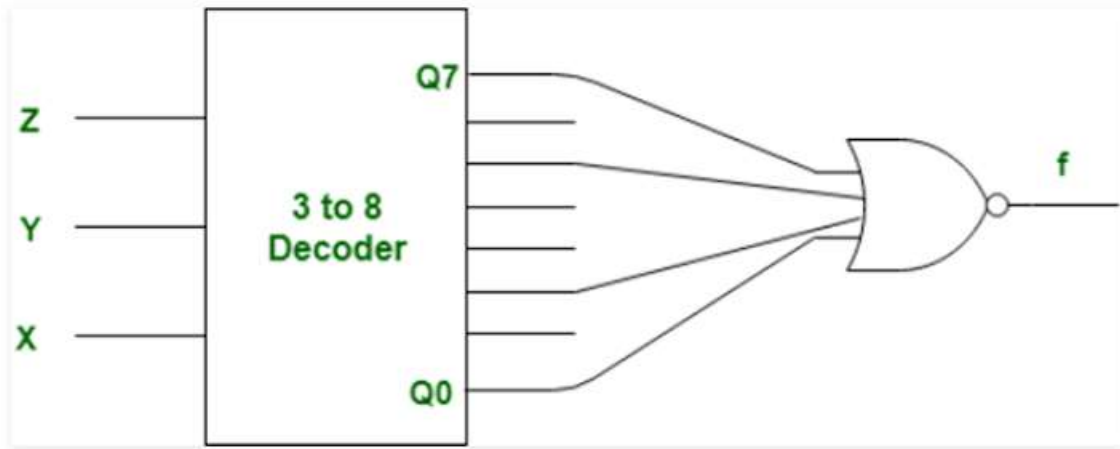What Boolean function does the circuit below realize ?



- ☐ B) $xz' + x'z$
- ☐ $xz + x'z'$
- ☒ $x'y' + yz$
- ☐ $xy + y'z'$

*


How many pulses are needed to change the contents of a 8-bit up counter from 10101100 to 00100111 (rightmost bit is the LSB)?

- ☐ 133
- ☒ 123
- ☐ 134
- ☐ 124



*

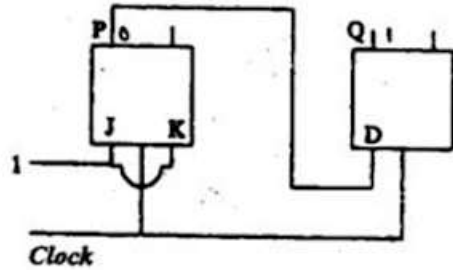
The following arrangement of master-slave flip flops has the initial state of P, Q as 0, 1 (respectively). After three clock cycles the output state P, Q is (respectively),



- ☒ 1, 0
- ☐ 0, 0
- ☐ 0, 1
- ☐ B) 1, 1



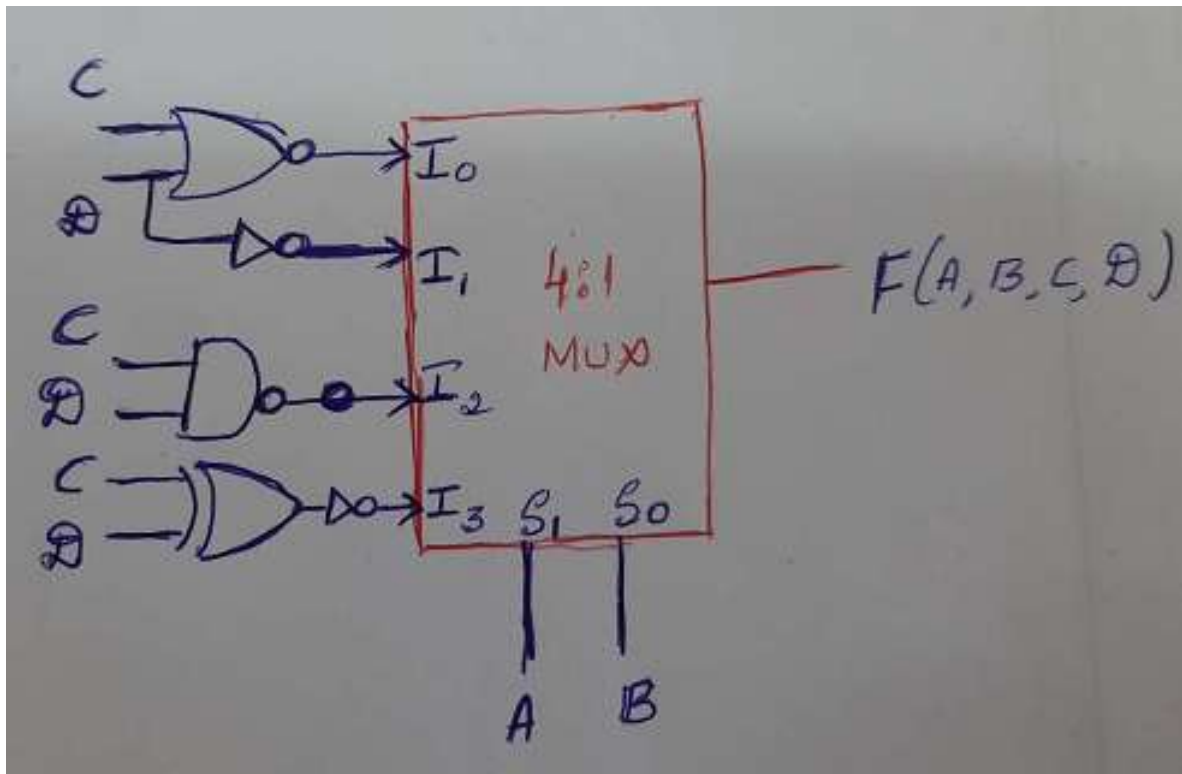The Boolean function realized by the logic circuit shown is *




- ☐ $F = \sum m(0, 4, 6, 11, 12, 13)$
- ☒ $F = \sum m(0, 4, 6, 9, 11, 12)$
- ☐ $F = \sum m(0, 4, 6, 10, 11, 12)$
- ☐ $F = \sum m(0, 4, 6, 11, 12, 15)$



*

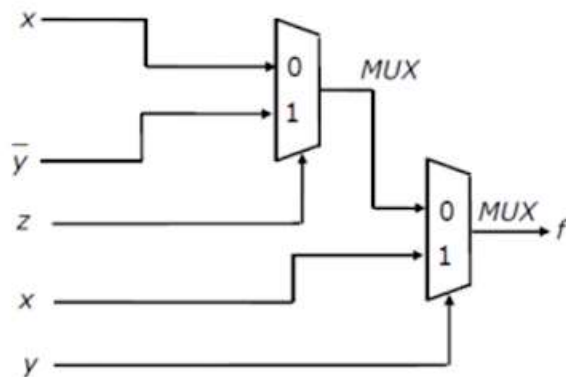Consider the circuit above. Which one of the following options correctly represents $f(x,y,z)$?




- ☐ $xz + xy' + y'z$
- ☐ $xy' + xy + y'z$
- ☒ $xz + xy + (yz)'$
- ☐ $xz' + xy + (yz)'$



*

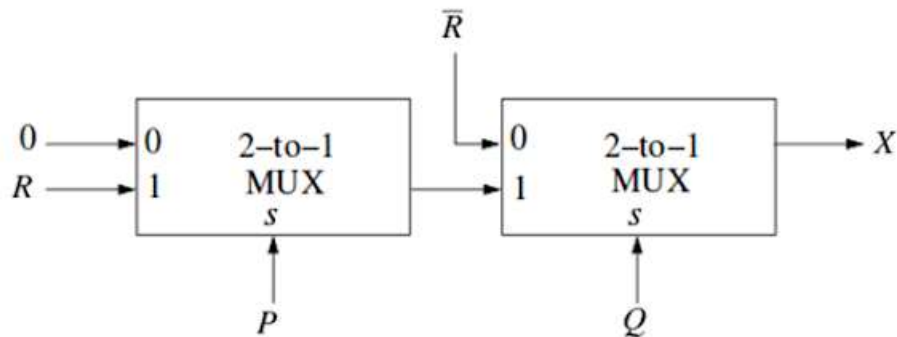Consider the two cascaded 2-to-1 multiplexers as shown in the figure.



The minimal sum of products form of the output X is

(A) $\bar{P}\bar{Q} + PQR$

(B) $\bar{P}Q + QR$

(C) $PQ + \bar{P}\bar{Q}R$

(D) $\bar{Q}\bar{R} + PQR$

☐ C

☒ D

☐ B

☐ A

An Asynchronous Counter is a *

☐ None of the above

☐ Parallel Counter

☐ Fast Counter


☒ Ripple Counter



Which of the following is a sequential circuit? *

- ☐ Decoder
- ☐ Full adder
- ☒ Counter
- ☐ Multiplexer

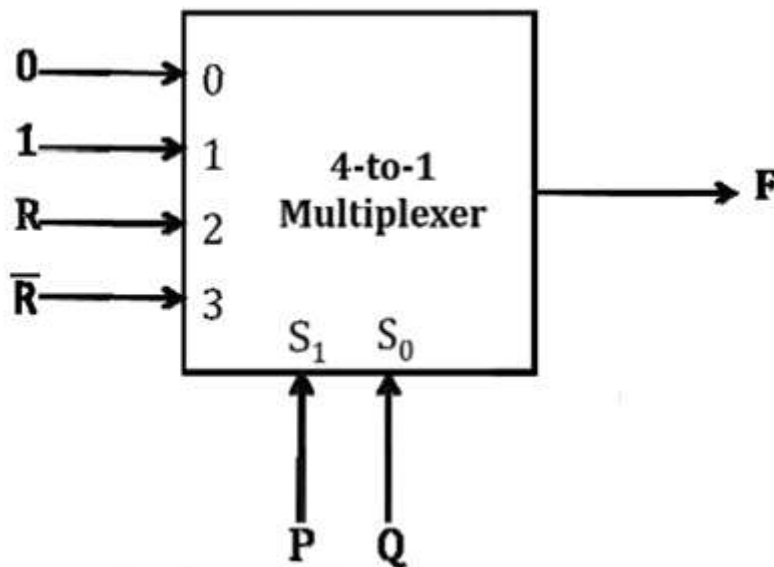The Boolean expression for the output F of the multiplexer shown below is *



- ☐ D) PQR'
- ☐ C) $P'QR + P'QR' + QR' + PQ'R$
- ☐ $P'Q + P'QR' + PQR' + PQ'R$
- ☒ $P'Q + QR' + PQ'R$



In Boolean algebra, rule $(X+Y)(X+Z) = *$

- ☐ XZ+Y
- ☐ XY+Z
- ☐ Y+XZ
- ☒ X+YZ

A combinational logic circuit which generates a particular binary word or number is *

- ☐ Decoder
- ☐ Encoder
- ☐ Demultiplexer
- ☒ Multiplexer

*

In a positive-edge-triggered JK flip-flop, if J and K both are high then the output will be _____ on the rising edge of the clock.

- ☐ Reset
- ☐ No change
- ☒ Toggle
- ☐ Set



*

What is the minimum number of NAND gates required to implement a 2-input EXCLUSIVE-OR function without using any other logic gate?

- ☒ 4
- ☐ 5
- ☐ 3
- ☐ 6

*

The Boolean function with the Karnaugh map is:


CD \ AB	AB			
	00	01	11	10
00	0	1	1	0
01	0	1	1	1
11	1	1	1	1
10	0	1	1	0

- ☒ $(A+C).D+B$
- ☐ $(A+D).C+B$
- ☐ $(A+C).B+D$
- ☐ $(A+B).C+D$



*

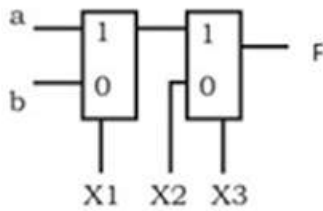The following circuit implements a two-input AND gate using two 2-1 multiplexers. What are the values of X_1 , X_2 , X_3 ?



- ☐ $X_1=a, X_2=0, X_3=b$
- ☒ $X_1=b, X_2=0, X_3=a$
- ☐ $X_1=a, X_2=b, X_3=1$
- ☐ $X_1=b, X_2=1, X_3=b$

Evaluate $(X \text{ xor } Y) \text{ xor } Y$? *

- ☐ All 1's
- ☒ X
- ☐ All 0's
- ☐ Y




*

Which of the following binary number is the same as its 2's complement?

- ☐ 0101
- ☐ 1001
- ☒ 1000
- ☐ 1010

*

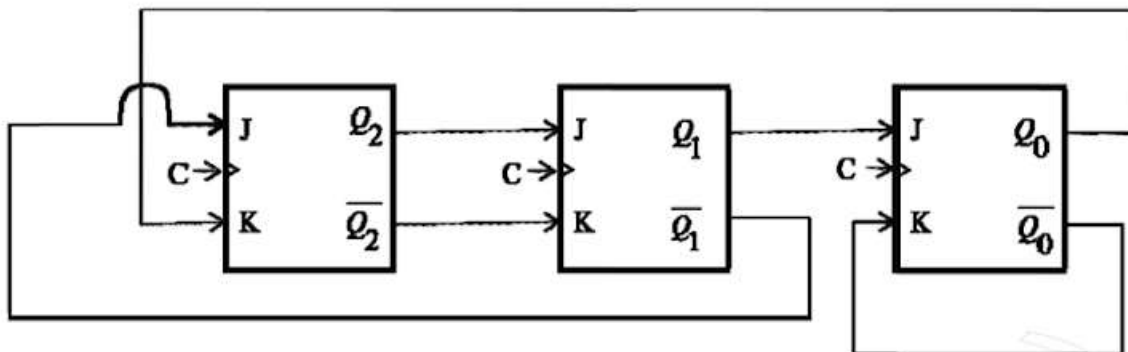The below sequential circuit is built using JK flip-flops is initialized with $Q_2Q_1Q_0 = 000$. The state sequence for this circuit for the next 3 clock cycle is




- ☒ 100, 110, 111
- ☐ 100, 011, 001
- ☐ 111, 110, 101
- ☐ 001, 010, 011



*

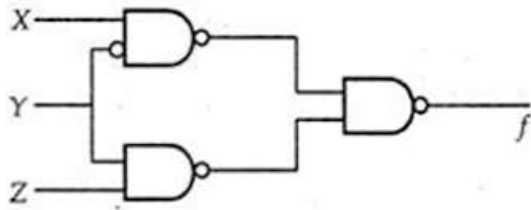Consider the following circuit. Which one of the following is TRUE?



- ☐ f is independent of Y
- ☒ None of X, Y, Z is redundant
- ☐ f is independent of X
- ☐ f is independent of Z

☒ Send me a copy of my responses.

[Back](#)[Submit](#)

Never submit passwords through Google Forms.

This form was created inside of Nitte Meenakshi Institute of Technology. [Report Abuse](#)

Google Forms

